
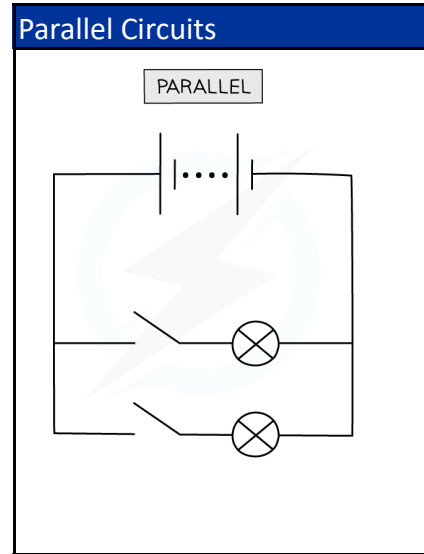


### Circuits

Circuit diagrams use standard symbols.

	switch (open)		lamp
	switch (closed)		fuse
	cell		voltmeter
	battery		ammeter
	diode		thermistor
	resistor		LDR
	variable resistor		LED

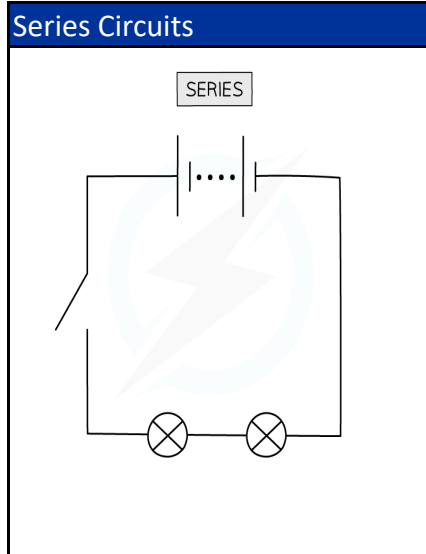

### Series and Parallel Circuits

	Series	Parallel
<b>Circuit</b>		
<b>Voltage</b>	$V_{in} = V_1 + V_2 + V_3$	$V_{in} = V_1 = V_2 = V_3$
<b>Current</b>	$I_{in} = I_1 = I_2 = I_3$	$I_{in} = I_1 + I_2 + I_3$
<b>Resistance</b>	$R_{total} = R_1 + R_2 + R_3$	$R_{total} < R_1 + R_2 + R_3$

### Resistance

Resistance is the **opposition to current**

**KEY**  
 = METAL ATOM  
 = FREE ELECTRON

FREE ELECTRONS COLLIDING WITH METAL ATOMS AS THEY FLOW TO THE RIGHT

20°C

IT IS HARDER FOR THE ELECTRONS TO FLOW (INCREASE IN RESISTANCE)

70°C

AS THE TEMPERATURE INCREASES THE ATOMS VIBRATE

### Power

- The **power transfer** in any circuit device is related to the **potential difference** across it and the **current** through it, and to the energy changes over time:
- power = potential difference  $\times$  current
- $(P = V I)$
- power = current  $^2 \times$  resistance
- $(P = I^2 R)$

Power (P): in watts (W)  
 potential difference (V): in volts (V)  
 Current (I): in amperes (A)  
 Resistance (R): in ohms ( $\Omega$ )

### Electricity in the Home

Most electrical appliances are connected to the mains using **three-core cable**. The insulation covering each wire is colour coded for easy identification:

- live wire** – brown
- neutral wire** – blue
- earth wire** – green and yellow stripes.

The **live wire** carries the **alternating potential difference** from the supply. The **neutral wire** completes the circuit. The **earth wire** is a safety wire to stop the appliance becoming live.

The **potential difference** between the **live wire** and earth (0 V) is about **230 V**. The **neutral wire** is at, or close to, earth potential (0 V). The earth wire is at 0 V, it only carries a current if there is a fault. A live wire may be **dangerous** even when a switch in the mains circuit is open.

**Figure 2** Inside a three-pin plug

Mains electricity is an ac supply. In the United Kingdom the domestic electricity supply has a frequency of 50 Hz and is about 230 V. Direct current flows in one direction only. Alternating current constantly changes direction.

### Magnetic fields

Use a compass to plot a magnetic field:  
 Magnetic field of the Earth and a magnet:

### Magnets

- Magnets**  
 (a) Magnets have a **north** and **south** pole.  

Opposite poles **attract**

Same poles **repel**
- (b) The magnetic field is strongest at the poles  
 Permanent – Always magnetic  
 Induced magnet – Can be turned on or off
- (c) **Electromagnets** can be turned on and off and are created by wrapping a coil of wire (solenoid) around an iron core.
- (d) **Electromagnets** can be strengthened by the 3Cs (larger CIRCUMFERENCE, more COILS, more CURRENT)

**Currents and Magnetism**  
 a) An **alternating magnetic** field can induce a **current**  
 b) An **alternating current** can induce a **magnetic field**